

BJT Amplifier

BJT Amplifier

Introduction

- The things you learned about **biasing a transistor** in the previous topic are now applied in this new topic where BJT circuits are used **a small-signal amplifiers**.
- The term **small-signal** refers to the use of signals that take up a relatively **small percentage** of an amplifier's **operational range**.
- Additionally, you will learn how to reduce an amplifier to an **equivalent dc and ac circuit** for easier analysis, and you will learn about multistage amplifiers.

BJT Amplifier

Amplifier Operation

Transistor AC Models

The Common-Emitter Amplifier


The Common-Collector Amplifier

The Common-Base Amplifier

Amplifier Operation

AC Quantities

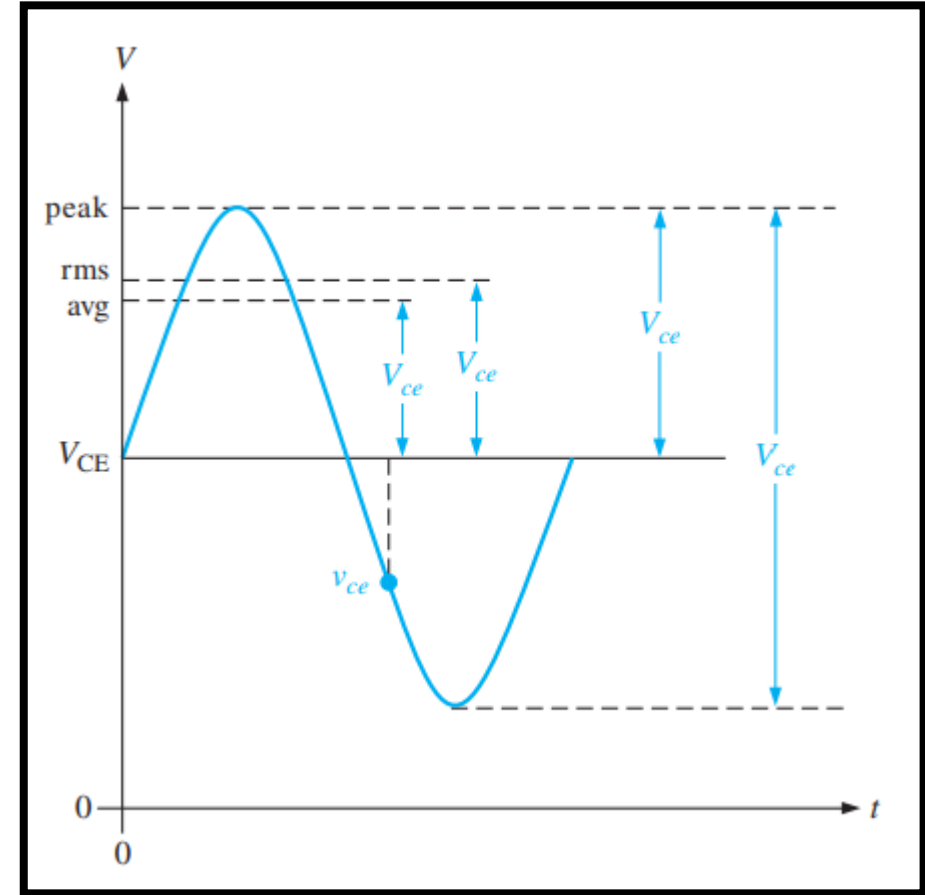
- *Lowercase italic* subscripts are used to indicate AC quantities.
- **rms** values are assumed unless otherwise stated.
- The figure illustrates these quantities for a specific voltage waveform.
- *Lowercase subscripts* are used to identify ac resistance value.
- rms: $\frac{1}{\sqrt{2}}$
- avg: $\frac{2}{\pi}$



Amplifier Operation

Linear Amplifier

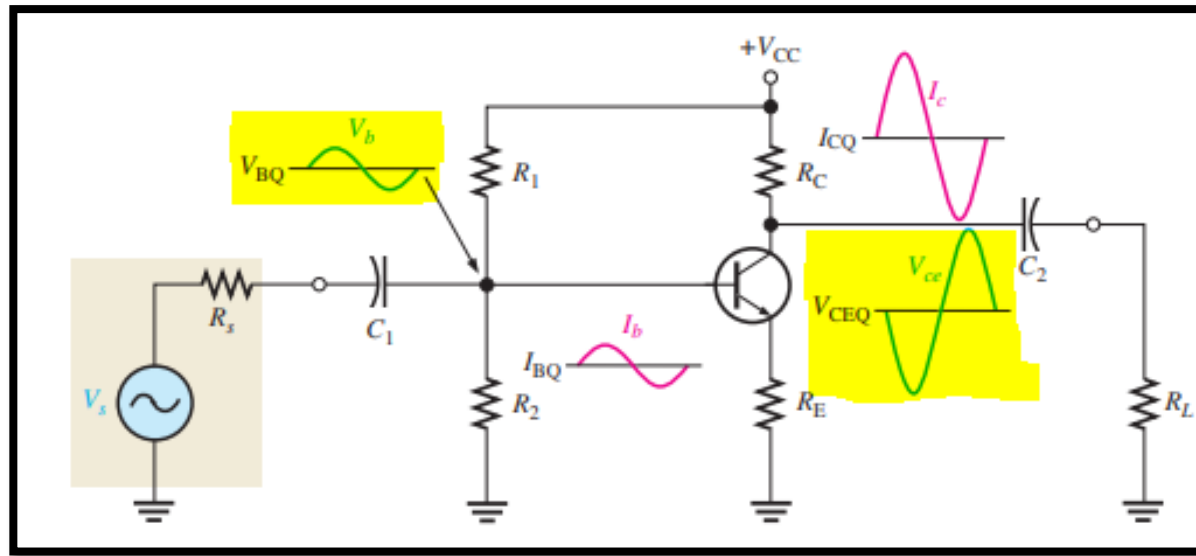- A linear amplifier provides **amplification** of a signal **without any distortion** so that the output signal is an exact amplified **replica** of the input signal.





- For the amplifier shown, notice that the voltage waveform is **inverted** between the input and output but has the **same shape**.

Amplifier Operation

AC Load line

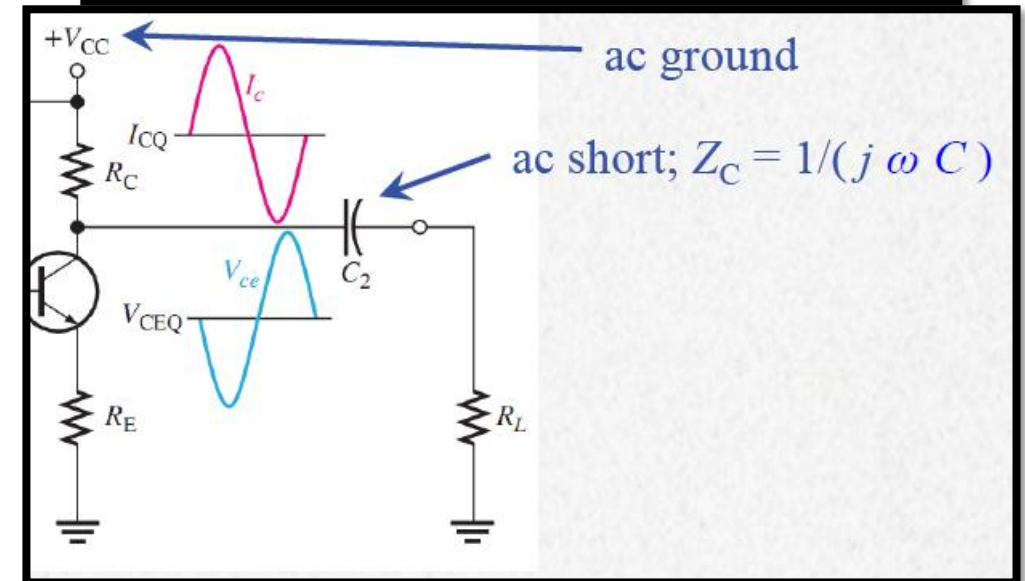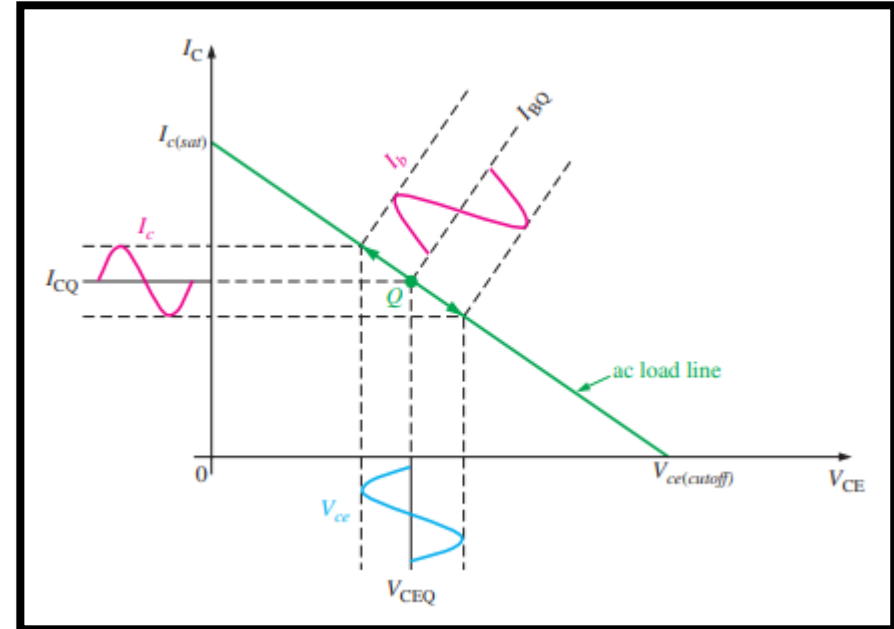- Operation of the **linear** amplifier can be illustrated using an **ac load line**.
- The ac load line is different than the dc load line because a **capacitor looks open to dc but effectively acts as a short to ac**.
- Thus the collector resistor R_C appears to be in **parallel** with the load resistor **RL**.



BJT Amplifier

Amplifier Operation


Transistor AC Models

The Common-Emitter Amplifier


The Common-Collector Amplifier

The Common-Base Amplifier

Transistor AC Model

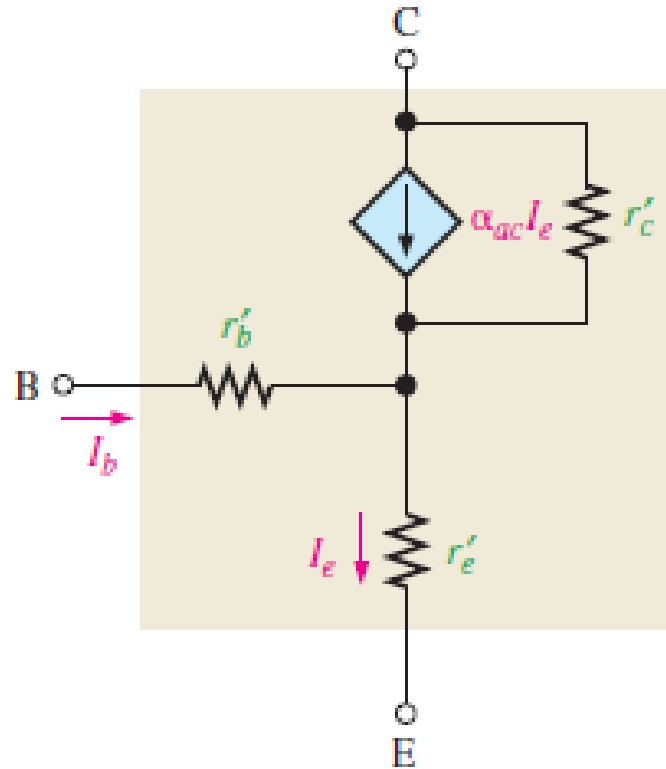

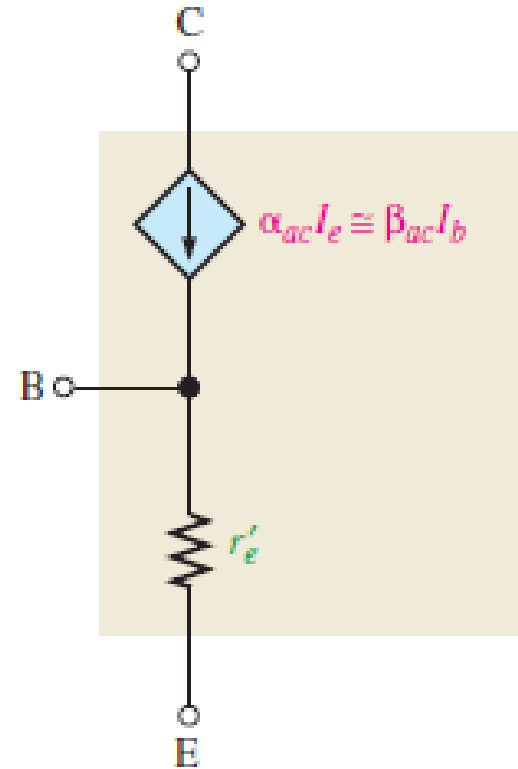(a) Generalized r -parameter model for a BJT



(b) Simplified r -parameter model for a BJT

▲ FIGURE 6-5


r -parameter transistor model.

Transistor AC Model

▼ TABLE 6-1

r parameters.

r PARAMETER	DESCRIPTION
α_{ac}	ac alpha (I_c/I_e)
β_{ac}	ac beta (I_c/I_b)
r'_e	ac emitter resistance
r'_b	ac base resistance
r'_c	ac collector resistance

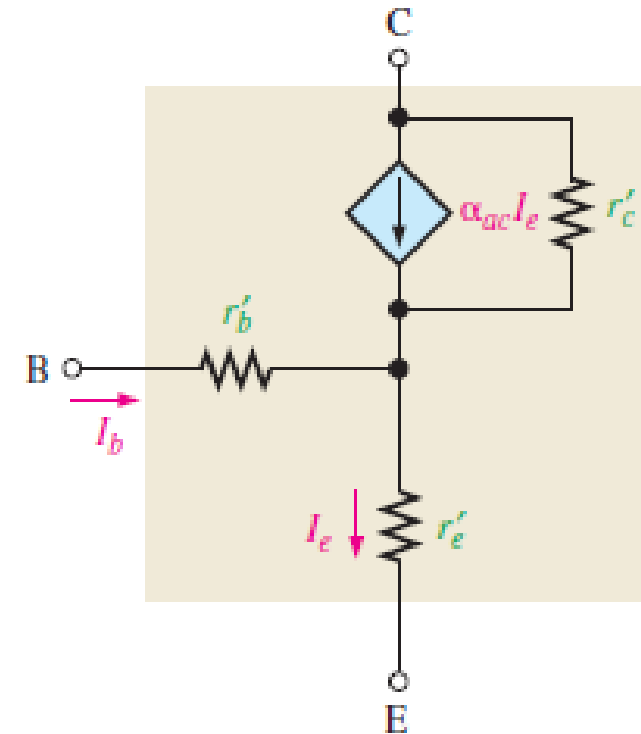


(a) Generalized r -parameter model for a BJT

Transistor AC Model

- The five **resistance parameters (r-parameters)** can be used for detailed analysis of a BJT circuit.
- For most analysis work, the simplified r-parameters give good results.
 - The simplified r-parameters are shown in relation to the transistor model.
 - An important r-parameter is r'_e . It appears as a small ac resistance between the base and emitter.

$$r'_e \cong \frac{25\text{mV}}{I_E}$$

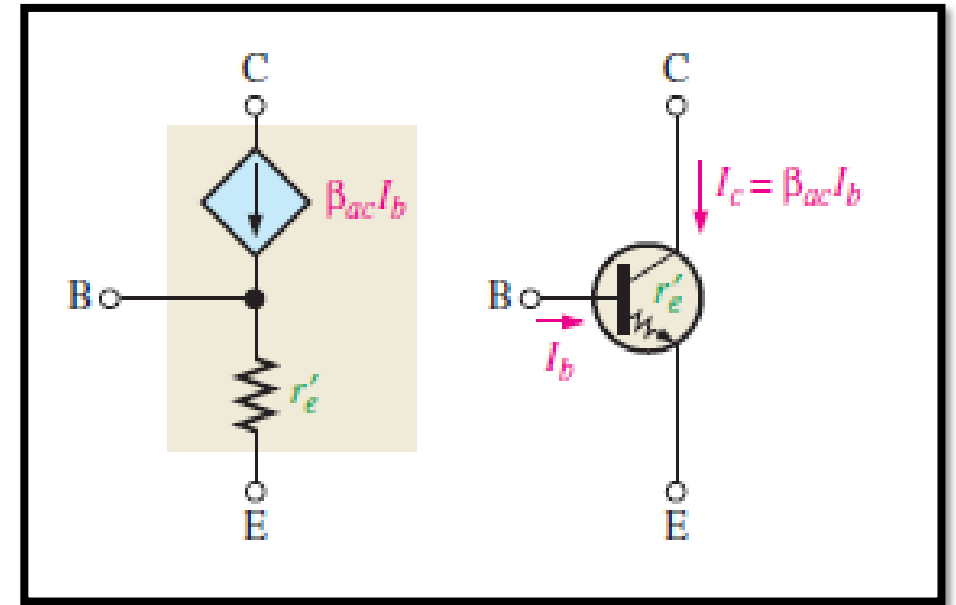assuming an abrupt junction between the n and p regions. and an ambient temperature of 20°C.



► **FIGURE 6-6**

Relation of transistor symbol to r-parameter model.

Example 1

- Determine the r_e' of a transistor that is operating with a dc emitter current of 2 mA.

- *Solution*

$$r_e' \cong \frac{25\text{mV}}{I_E} = \frac{25\text{mV}}{2\text{mA}} = 12.5\Omega$$

BJT Amplifier

Amplifier Operation

Transistor AC Models

The Common-Emitter Amplifier

The Common-Collector Amplifier


The Common-Base Amplifier

The Common-Emitter Amplifier

Introduction

- In the common-emitter (CE) amplifier, the input signal is applied to the base and the inverted output is taken from the collector.
- The emitter is common to ac input & output signals.
- CE amplifiers exhibit high voltage gain and high current gain.

The Common-Emitter Amplifier

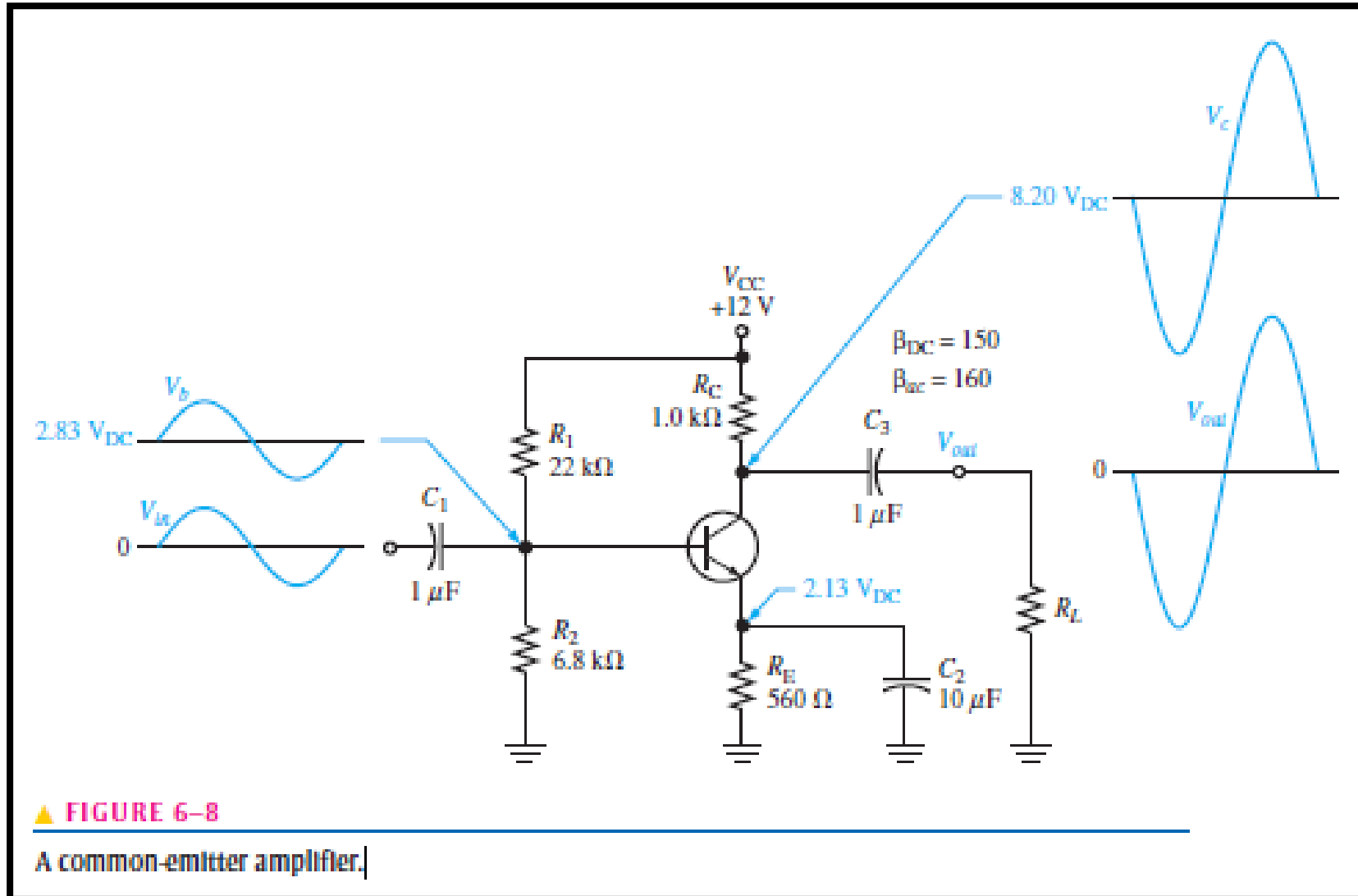

The Common-Emitter Amplifier

DC Analysis

- To analyze the amplifier in the previous figure, a dc equivalent circuit is developed by removing the coupling and bypass **capacitors** because they appear **open** as far as the dc bias is concerned.

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(6.8 \text{ k}\Omega)(22 \text{ k}\Omega)}{6.8 \text{ k}\Omega + 22 \text{ k}\Omega} = 5.19 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{6.8 \text{ k}\Omega}{6.8 \text{ k}\Omega + 22 \text{ k}\Omega} \right) 12 \text{ V} = 2.83 \text{ V}$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta_{DC}} = \frac{2.83 \text{ V} - 0.7 \text{ V}}{560 \Omega + 34.6 \Omega} = 3.58 \text{ mA}$$


$$I_C \cong I_E = 3.58 \text{ mA}$$

$$V_E = I_E R_E = (3.58 \text{ mA})(560 \Omega) = 2 \text{ V}$$

$$V_B = V_E + 0.7 \text{ V} = 2.7 \text{ V}$$

$$V_C = V_{CC} - I_C R_C = 12 \text{ V} - (3.58 \text{ mA})(1.0 \text{ k}\Omega) = 8.42 \text{ V}$$
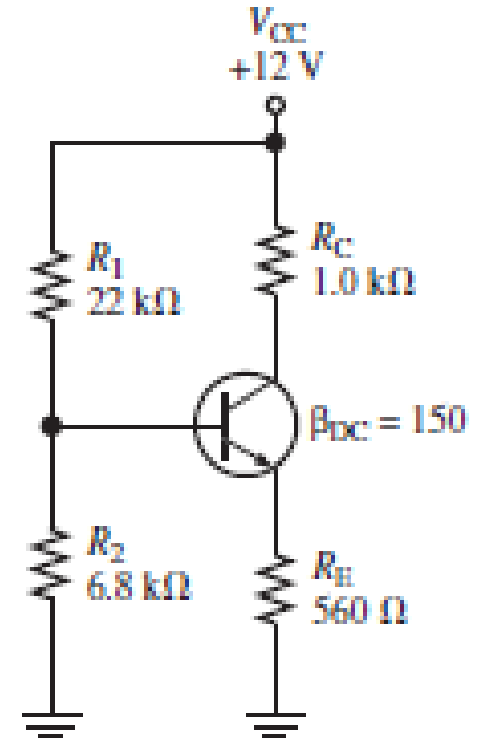
$$V_{CE} = V_C - V_E = 8.42 \text{ V} - 2 \text{ V} = 6.42 \text{ V}$$



▲ FIGURE 6-9

DC equivalent circuit for the amplifier in Figure 6-8.

BJT Amplifier

Amplifier Operation

Transistor AC Models

The Common-Emitter Amplifier

The Common-Collector Amplifier


The Common-Base Amplifier

The Common-Collector Amplifier

Introduction

- The common-collector (CC) amplifier is usually referred to as an emitter-follower (EF).
- The **input is applied to the base** through a coupling capacitor, and the **output is at the emitter**.
- The **voltage gain** of a CC amplifier is approximately **1**, and its main advantages are its high input resistance and current gain.

The Common-Collector Amplifier

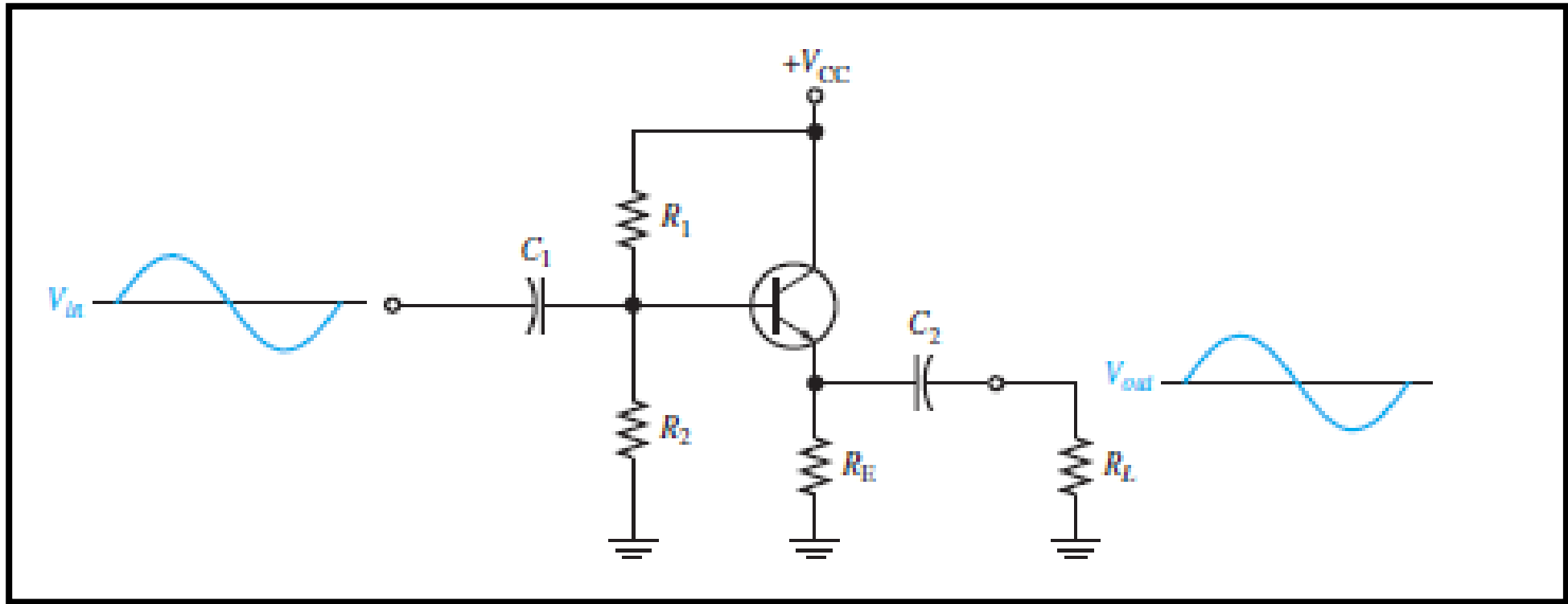

► **FIGURE 6-25**

Emitter-follower with voltage-divider bias.

BJT Amplifier

Amplifier Operation

Transistor AC Models

The Common-Emitter Amplifier

The Common-Collector Amplifier


The Common-Base Amplifier

The Common-Base Amplifier


Introduction

- The common-base (CB) amplifier provides high voltage gain with a maximum current gain of 1.
- Since it has a low input resistance, the CB amplifier is the most appropriate type for certain applications where sources tend to have very low-resistance outputs.
- The base is the common terminal and is at ac ground because of capacitor C_2 .
- The **input signal** is capacitively coupled to the **emitter**. The **output** is capacitively coupled from the **collector** to a load resistor.

The Common-Base Amplifier

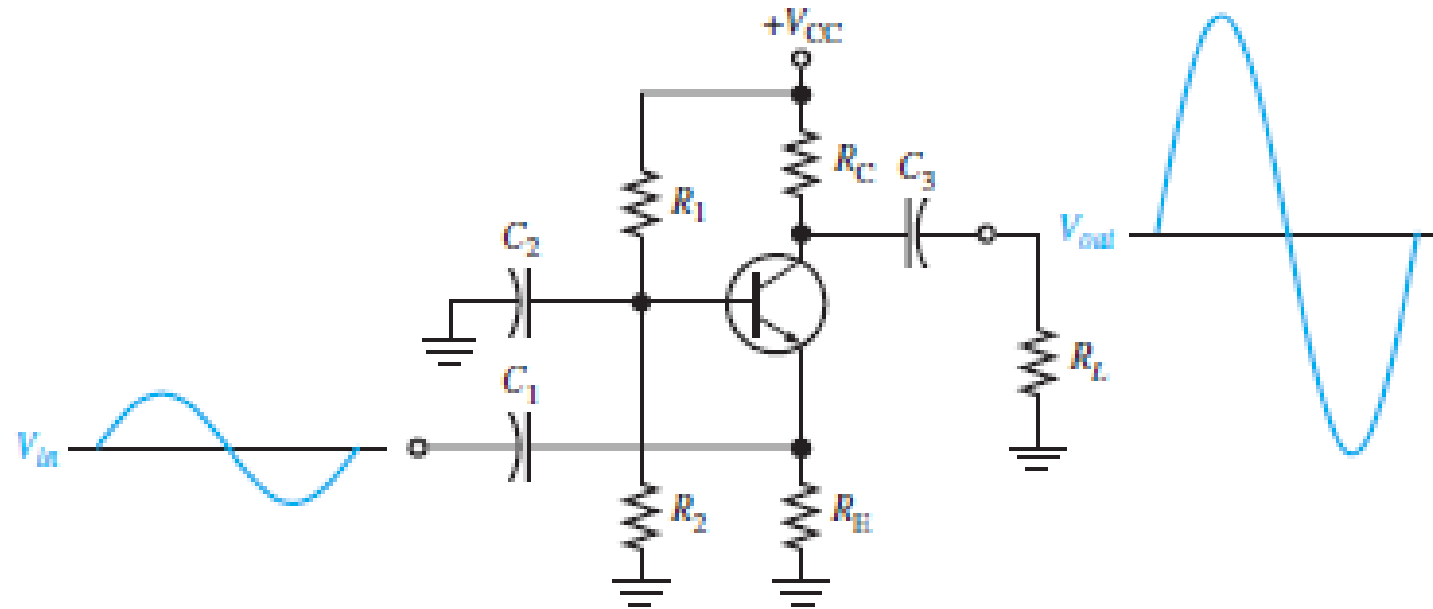

(a) Complete circuit with load

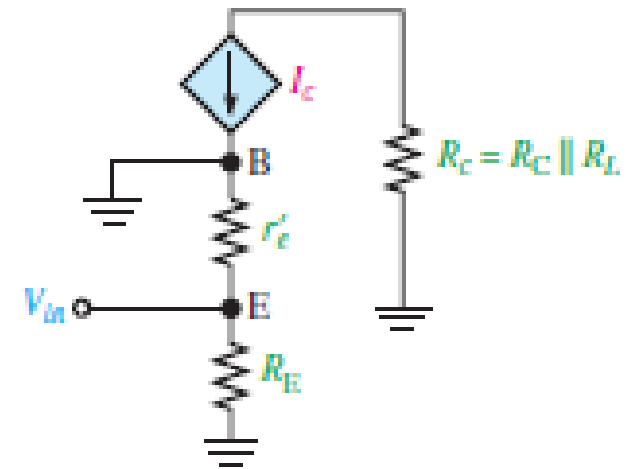

(b) AC equivalent model

▲ FIGURE 6-31

Common-base amplifier with voltage-divider bias.